XYZ International School of Physics

2547 Broadway Street, North Charleston, South Carolina 29420

PHY0101 - ELECTRICITY Test Paper

1.5 hours

30 marks

INSTRUCTIONS

- Don't Copy
- You can use calculators
- Check the time in between

SECTION - A

Answer any three of the following multiple choice questions.

- Each right answer will secure you 1.5 marks.
- There is no negative marking.

Question 1: What is the resistance of the given carbon resistor? *Hint: Use the colour code for carbon resistors.* (1.5 marks)



Figure 1

(a) 10 k Ω	(b) 1 k Ω
(c) 100 Ω	(d) 100 k Ω

Question 2: Find the equivalent resistance in both cases?

 $\begin{array}{c} 3 \text{ ohm} \\ & & & & & & & \\ & & & & & & & \\ & & & & & & & \\ & & & & & & & \\ & & & & & & & \\ & & & & & & & \\ & & & & & & & \\ & & & & & & & \\ & & & & & & & \\ & & & & & & & \\ & & & & & & & \\ & & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ &$

- (a) 1 Ω , 2 Ω (b) 2 Ω , 1 Ω (c) 0.33 Ω , 0.5 Ω
- (d) 0.5Ω , 0.33Ω

Question 3: The Ohm's law is given by the following equation. What can you say about the quantity \mathbb{R} ? (1.5 marks)

$$V = IR$$

(a) Always Constant
(b) Constant at times; changes with physical conditions
(c) Variable
(d) Infinite

Question 4: In parallel combination of n cells, we obtain

(a) more voltage	(b) more current
(c) less voltage	(d) less current

SECTION - B

Write answers to the following questions in 1 or 2 sentences.

- Answer all questions.
- Marks will be deducted for exceeding the prescribed word limit.

Question 1: State Ohm's Law.

Question 2: What is an electric fuse?

(1.5 marks)

(1.5 marks)

(1 mark)

(1 mark)